

2006–11–07

Uppgift 12.4 (fig1)

$$u_c(t) = 5 \cos(10^4 t - 45^\circ) \text{ V}$$

$$\omega = 10^4 \text{ rad/s}$$

$$C = 100 \mu\text{F}$$

Antag sinusformat stationärtillstånd.

$j\omega$ -transformera kretsen (fig2).

$$U_C = 5 / \underline{-45^\circ}$$

$$\omega L = 10^4 \cdot 10^{-4} = 1$$

$$\frac{1}{\omega C} = \frac{1}{10^4 \cdot 100 \cdot 10^{-6}} = 1$$

$$I_C = \frac{U_C}{\frac{1}{i\omega C}} = \frac{U_C}{-i} = i U_C = 1 / \underline{90^\circ} \cdot 5 / \underline{-45^\circ} = 5 / \underline{45^\circ} = \frac{5}{\sqrt{2}} (1 + i)$$

$$U_0 = I_C \left(R + \frac{1}{i\omega C} \right) = I_C R + U_C = I_C (1 - i) = 5 / \underline{45^\circ} \sqrt{2} / \underline{-45^\circ} = 5\sqrt{2} / \underline{0^\circ}$$

$$I_L = \frac{U_0}{i\omega L} = \frac{5\sqrt{2}}{i} = 5\sqrt{2} / \underline{-90^\circ}$$

$$I = I_L + I_C = -i 5\sqrt{2} + \frac{5}{\sqrt{2}} + i \frac{5}{\sqrt{2}} = \frac{5}{\sqrt{2}} - i \frac{5}{\sqrt{2}} = 5 / \underline{-45^\circ}$$

$$U_R = I_C \cdot R = 5 / \underline{45^\circ}$$

Svar: $u_0(t) = 5\sqrt{2} \cos(10^4 t) \text{ V}$, $i(t) = 5 \cos(10^4 t - 45^\circ) \text{ A}$.

Vi räknade även 12.5, 12.8 och 12.9; 6.2