

2006–12–13

Uppgift C6 (fig1)

I aktiva området $u_{BE_1} = u_{BE_2} = u_{BE} = 0.7 \text{ V}$.

T_1 : $\beta_1 = 100$, T_2 : $\beta_2 = 50$.

$$I_C = \beta I_B$$

Teckna kretsekvationer:

$$\begin{aligned} R_2 I_2 &= I_{B2} R_3 + u_{BE} + u_{BE} - I_E R_E \\ -I_{E1} &= I_{C1} + I_{B1} = I_{B1}(1 + \beta_1) = (I_{B2} + I_{C2})(1 + \beta_1) = I_{B2}(1 + \beta_2)(1 + \beta_1) \\ R_2 I_2 &= I_{B2}(R_3 + R_E(1 + \beta_2)(1 + \beta_1)) + 2 u_{BE} \\ E &= R_1 I_1 + R_2 I_2 = [I_1 = I_{B2} + I_2] = I_2(R_1 + R_2) + I_{B2} \cdot R_1 \\ \Rightarrow I_2 &= \frac{E - I_{B2} R_1}{R_1 R_2} \end{aligned}$$

ger

$$\begin{aligned} \frac{R_2 E}{R_1 + R_2} &= I_{B2} \left(R_3 + R_E(1 + \beta_1)(1 + \beta_2) + \frac{R_1 R_2}{R_1 + R_2} \right) + 2 u_{BE} \\ I_{B2} &= \frac{\frac{R_2 E}{R_1 + R_2} - 2 u_{BE}}{R_3 + R_E(1 + \beta_1)(1 + \beta_2) + \frac{R_1 R_2}{R_1 + R_2}} = \dots = 1.94 \mu\text{A} \end{aligned}$$

Resten av strömmarna:

$$\begin{aligned} I_{C2} &= \beta_2 \cdot I_{B2} = \dots = 96.8 \mu\text{A} \\ I_{B1} &= I_{B2} + I_{C2} = \dots = 98.8 \mu\text{A} \\ I_{C1} &= \beta_1 \cdot I_{B1} = \dots = 9.88 \text{ mA} \\ I_{E1} &= -I_{B1} - I_{C1} = -9.98 \text{ mA} \\ I_2 &= \dots = 0.259 \text{ mA} \\ I_1 &= I_2 + I_{B2} = \dots = 0.261 \text{ mA} \\ u_1 &= E - I_{C1} \cdot R_C = \dots = 14.1 \text{ V} \\ u_2 &= -I_{E1} \cdot R_E = \dots = 1.0 \text{ V} \end{aligned}$$

Uppgift D3 (fig2)

Transistor BC167B, arbetspunkt $I_C = 1 \text{ mA}$, $u_{CE} = 10 \text{ V}$. Ur datablad fås:

Vid $I_C = 2 \text{ mA}$, $u_{CE} = 5 \text{ V}$	Korrektion, $I_C = 1 \text{ mA}$	Korrektion $u_{CE} = 10 \text{ V}$
$h'_{11} = 4.5 \text{ k}\Omega$	1.8	1.1
$h'_{12} = 2 \cdot 10^{-4}$	1.4	0.92
$h'_{21} = 330$	0.93	1.1
$h'_{22} = 30 \mu\text{S}$	0.63	0.72

Multipluera nominella värden med korrektionsfaktorer.

$$\begin{cases} h_{11} = 8.9 \text{ k}\Omega \\ h_{12} = 2.6 \cdot 10^{-4} \\ h_{21} = 338 \\ h_{22} = 14 \mu\text{S} \end{cases}$$

Småsignalschema (fig3).

Inresistans:

$$R_{\text{in}} = \frac{u}{i_{\text{in}}} = \frac{u}{i_b}$$

$$u = i_b \cdot h_{11} + h_{12} u_{\text{ce}} + i_1 R_E \quad (1)$$

$$i_1 R_E + i_2 \cdot \frac{1}{h_{22}} = 0 \implies i_2 = -i_1 R_E h_{22} \quad (2)$$

$$i_1 = i_b(1 + h_{21}) + i_2 = i_b(1 + h_{21}) - i_1 R_E h_{22} \implies i_1 = \frac{i_b(1 + h_{21})}{1 + R_E h_{22}} \quad (3)$$

$$u_{\text{ce}} + u_{\text{ut}} = 0, \quad u_{\text{ut}} = R_E i_1$$

$$u_{\text{ce}} = -u_{\text{ut}} = -i_1 R_E$$

Ur (1):

$$u = i_b h_{11} - i_1 h_{12} R_E + i_1 R_E = i_b h_{11} + i_1 R_E (1 - h_{12})$$

$$u = i_b h_{11} + i_b \frac{R_E(1 - h_{12})(1 + h_{21})}{1 + R_E h_{22}}$$

$$R_{\text{in}} = \frac{u}{i_b} = h_{11} + \frac{R_E(1 - h_{12})(1 + h_{21})}{1 + R_E h_{22}} = \dots = 409 \text{ k}\Omega$$

Utresistans:

Nollställ oberoende källor ($u_{\text{in}} = 0$). Applicera spänning på utgången, u_{ut} . Beräkna resulterande ström, i_{ut} . $R_{\text{ut}} = u_{\text{ut}}/i_{\text{ut}}$.

(fig4)

KCL:

$$i_{\text{ut}} = i_1 - i_b(1 + h_{21}) - i_2$$

KVL:

$$i_b(R_g + h_{11}) + u_{\text{ce}} h_{12} + i_1 R_E = 0$$

$$u_{\text{ce}} = -i_1 R_E$$

$$\implies i_b = -i_1 \frac{1 - h_{12}}{h_{11} + R_g}$$

$$i_2 \cdot \frac{1}{h_{22}} + i_1 R_E = 0$$

$$i_2 = -i_1 R_E h_{22}$$

$$i_{\text{ut}} = i_1 \left(1 + \frac{R_E}{h_{11} + R_g} (1 + h_{21})(1 - h_{12}) + R_E h_{22} \right)$$

$$u_{\text{ut}} = i_1 \cdot R_E$$

$$R_{\text{ut}} = \frac{u_{\text{ut}}}{i_{\text{ut}}} = \frac{R_E}{1 + R_E h_{22} + \frac{R_E}{h_{11} + R_g} (1 + h_{21})(1 - h_{12})} = \dots = 29 \Omega$$